IBM ASSIGNMENT-I

TEAM ID : PNT2022TMID26639


NAME: ANBU A

ROLL NO: 212919106008

Create a circuit with Piezo alarm, PIR Sensor, TMP Sensor with below functionalities:

- Alarm should sound in one manner if temp is above 60C
- Alarm should sound with another frequency if motion is detected in PIR Sensor.

CIRCUIT LAYOUT:

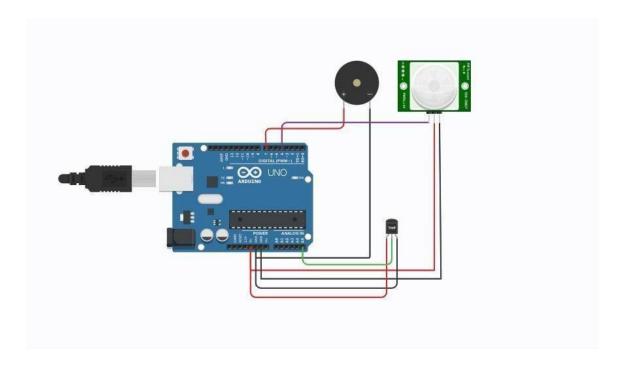


CODE:

```
// C++ code
//
void setup()
 Serial.begin (9600); pinMode(4,
 INPUT); pinMode(7,OUTPUT);
 pinMode(A5,INPUT);
}
void loop()
 int motion = digitalRead(4); if
 (motion==1){}
 Serial.println("Motion detected");
 tone (7,200); delay(350);
 }
 else{
  Serial.println("No Motion");
  noTone(7);
 double data=analogRead(A5);
 double n=data/1024; double
 volt=n*5; double off=volt-0.5;
 double temperature=off*100; if
 (temperature>59.99){
 Serial.print("Temperature data:");
 Serial.println(temperature); tone(7,1000);
 delay(350);
```

```
else
    Serial.print("Temperature data: "); Serial.println(temperature);
    noTone(7);
}
```

OUTPUT:

PASSIVE INFRARED SENSOR:

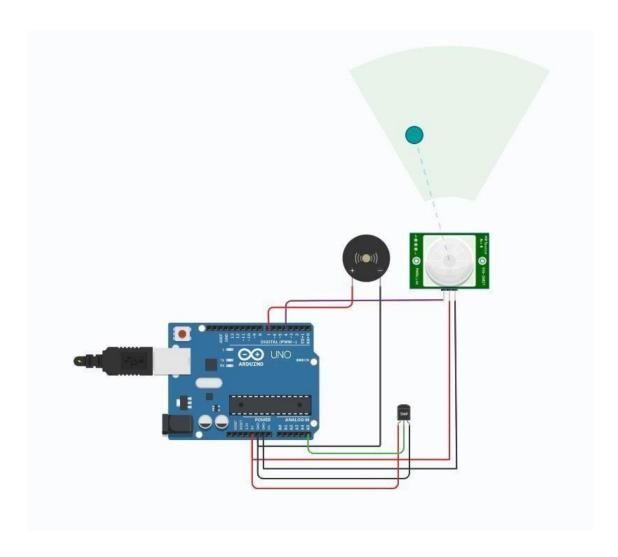

TEMPERTURE SENSOR (AT 60°C):

